
www.ecenacademy.com

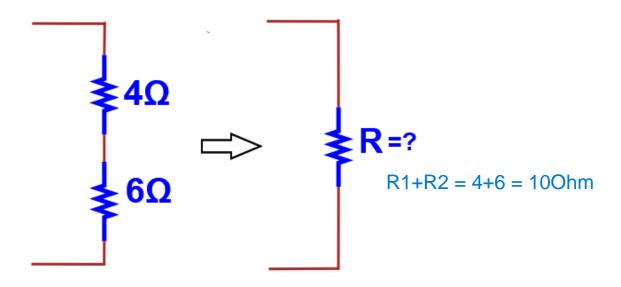

## <u>Electrical Problem – 41</u>

- 1. Do not discuss with any one while solving the problems
- 2. Do not use internet while solving the problems
- 3. Do not use books while solving the problems
- 4. Do not try to copy from others
- 5. Do the problems in an easy way.




www.ecenacademy.com (91) 97908 73099



## <u>Electrical Problem – 42</u>

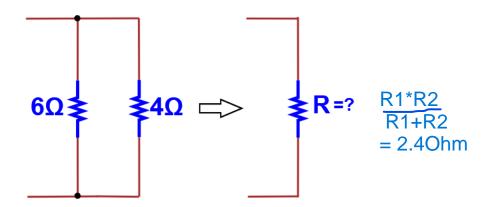- 1. Do not discuss with any one while solving the problems
- 2. Do not use internet while solving the problems
- 3. Do not use books while solving the problems
- 4. Do not try to copy from others
- 5. Do the problems in an easy way.




www.ecenacademy.com



### **Electrical Problem – 43**

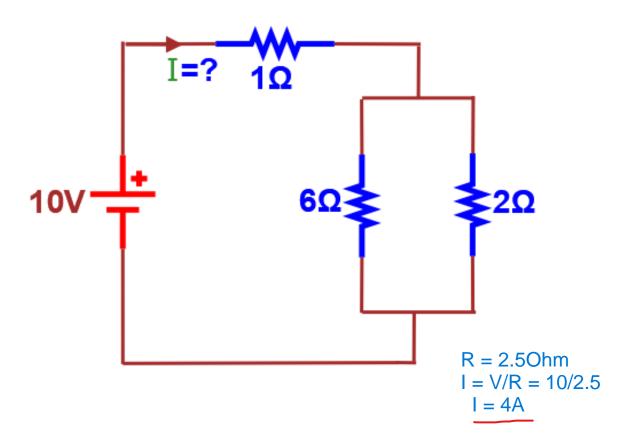- 1. Do not discuss with any one while solving the problems
- 2. Do not use internet while solving the problems
- 3. Do not use books while solving the problems
- 4. Do not try to copy from others
- 5. Do the problems in an easy way.




www.ecenacademy.com (91) 97908 73099



### **Electrical Problem – 44**

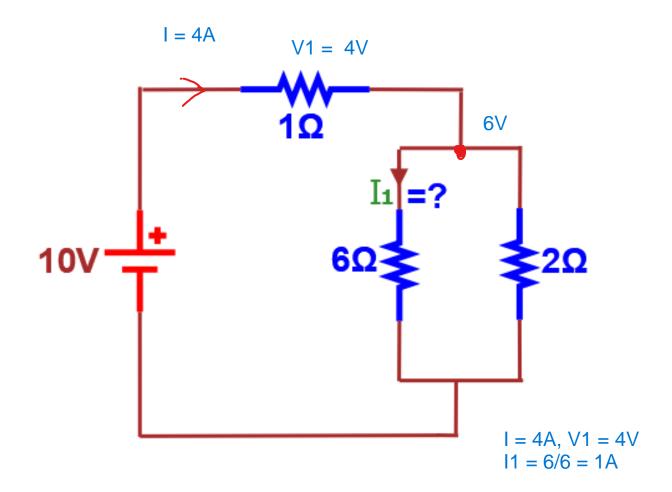- 1. Do not discuss with any one while solving the problems
- 2. Do not use internet while solving the problems
- 3. Do not use books while solving the problems
- 4. Do not try to copy from others
- 5. Do the problems in an easy way.




www.ecenacademy.com



### **Electrical Problem – 45**

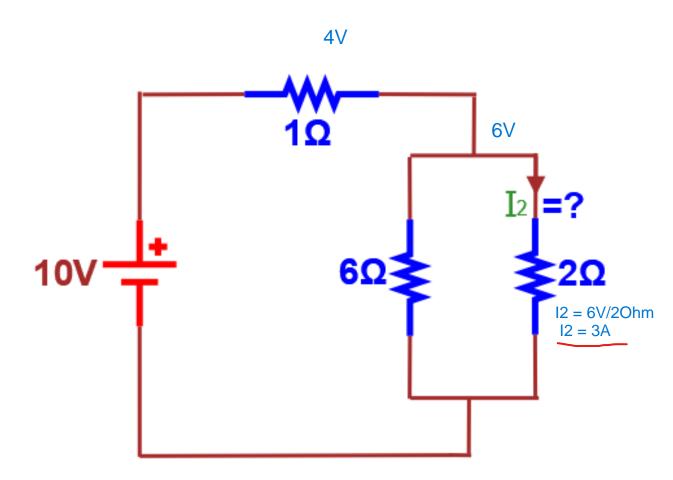- 1. Do not discuss with any one while solving the problems
- 2. Do not use internet while solving the problems
- 3. Do not use books while solving the problems
- 4. Do not try to copy from others
- 5. Do the problems in an easy way.




www.ecenacademy.com (91) 97908 73099



### **Electrical Problem – 46**

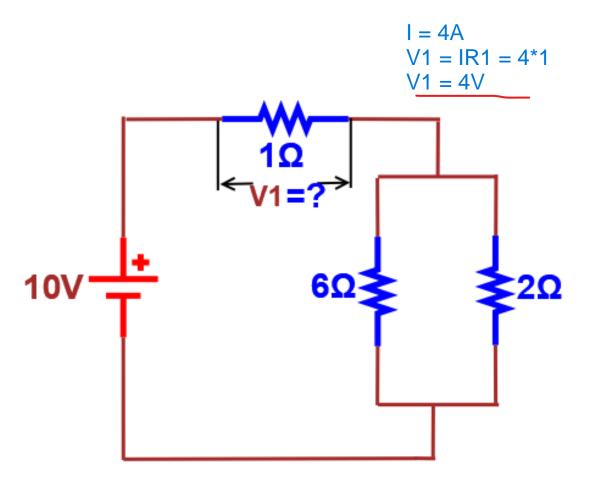- 1. Do not discuss with any one while solving the problems
- 2. Do not use internet while solving the problems
- 3. Do not use books while solving the problems
- 4. Do not try to copy from others
- 5. Do the problems in an easy way.




www.ecenacademy.com (91) 97908 73099



### **Electrical Problem – 47**

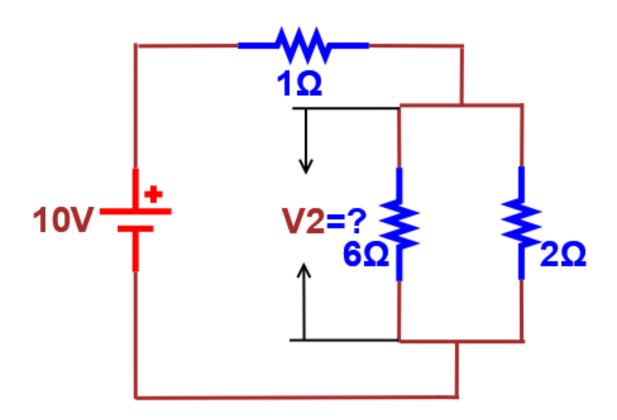- 1. Do not discuss with any one while solving the problems
- 2. Do not use internet while solving the problems
- 3. Do not use books while solving the problems
- 4. Do not try to copy from others
- 5. Do the problems in an easy way.




$$I = 4A, V1 = 4V$$
  
 $V2 = V-V1 = 10V-4V$   
 $V2 = 6V$ 

www.ecenacademy.com



### **Electrical Problem – 48**

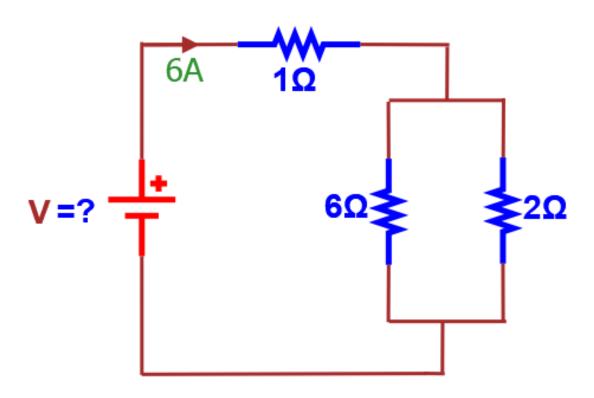- 1. Do not discuss with any one while solving the problems
- 2. Do not use internet while solving the problems
- 3. Do not use books while solving the problems
- 4. Do not try to copy from others
- 5. Do the problems in an easy way.






www.ecenacademy.com



### **Electrical Problem – 49**

### Instructions:

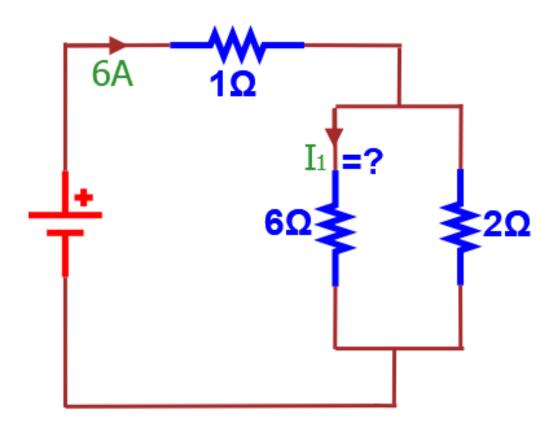- 1. Do not discuss with any one while solving the problems
- 2. Do not use internet while solving the problems
- 3. Do not use books while solving the problems
- 4. Do not try to copy from others
- 5. Do the problems in an easy way.



I =6A, R = 2.5Ohm, V = 15V V1 = 6V, V2 = 9V I1 = 9V/6Ohm = 1.5A




www.ecenacademy.com

**6** (91) 97908 73099

### **Electrical Problem – 50**

#### Instructions:

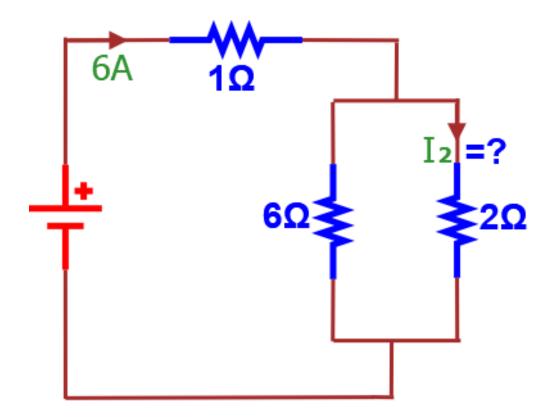- 1. Do not discuss with any one while solving the problems
- 2. Do not use internet while solving the problems
- 3. Do not use books while solving the problems
- 4. Do not try to copy from others
- 5. Do the problems in an easy way.



I = 6A , R = 2.5Ohm, V = 15V, V1 = 6V , V2 = 9V , I2= 9/2 = 4.5A